

DLD LAB – Experiment #4 - Accelerator and Wrappers


Ali Ghahari 810100201

Mohammad Sadeghi 810100175

Introduction

System on Chip is an integrated circuit that integrates multiple components. The main core of a SoC is a processor that handles different computational tasks. In addition to the processor, the system includes memory, Input/output ports, and accelerators. Accelerators are dedicated computation units that usually execute one specific task. This single task needs a smaller and less complicated datapath which leads to a high frequency. However, CPUs in which millions of operations must be executed within a fixed time interval have low frequency of operation. To increase the speed of a SOC, hardware accelerators are usually embedded in the system. The processor will dispute some of its tasks to the hardware accelerator. During this time, the accelerator performs several of the same or different operations and stores the result values in a memory. The CPU will access these results when it finishes its tasks. The focus of this experiment is on accelerators and how to integrate them into a SOC

Figure 1: Block diagram of a typical integrated circuit

 


When the CPU needs to compute an exponential value, because of the higher estimation speed of the accelerator it asks the exponential hardware accelerator to complete this task. In this way, the CPU can complete other software tasks in parallel. Before starting the computation, the CPU should send a data from memory to the accelerator. This data will be stored in a buffer

inside the accelerator. When transferring is finished, the CPU initiates the accelerator for an N-round exponential estimation. CPU uses its address bus for initiating a component. By decoding the address bus through an address logic as shown in figure 1, the accelerator will have its *start* signal issued when needed.


Exponential Engine

The accelerator that we are going to use is an exponential circuit. As Figure 2 shows, this module receives a 16-bit input *x* and generates a 16-bit output *Fractionalpart* and 2-bit *Integerpart*. Remember that the *x* value fits between zero and one. The accelerator starts working with a complete pulse on signal *start* and when the computation is completed signal *done* will be sent to the processor to aware it.

Figure 2: Block diagram of exponential accelerator

 


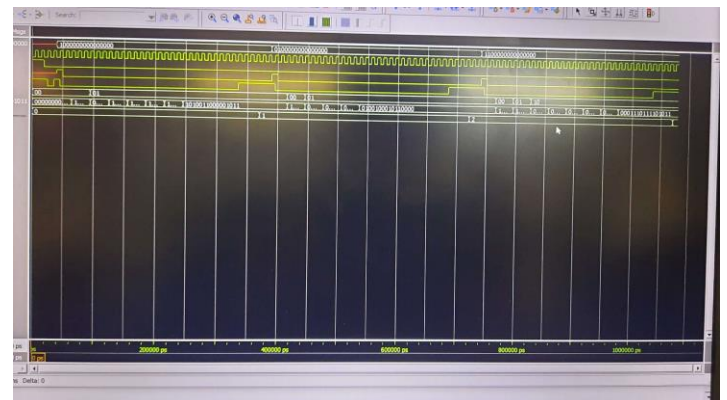For clock generation for this module we need to be aware of the maximum frequency of this accelerator. First we running Modelsim simulation of module, write a testbench for this design with three different values for input *x*.



As you can see we have three value for x and in three times done signal become 1.

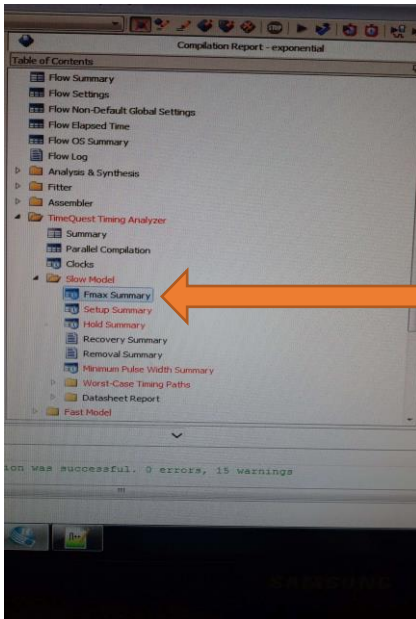In next step we Synthesize this design in Quartus II Software. After synthesizing the design, we can find out the maximum frequency of this accelerator by referring to the Timing Analyzer reports in the Quartus synthesis tool:



As in this part we can find maximum frequency of accelerator:

	Fmax	Restricted Fmax	Clock Name	Note
1	109.39 MHz	109.39 MHz	clk	

Exponential Accelerator Wrapper

One of the applications that makes use of such multi-value exponential calculation is an activation function in Deep Neural Networks (DNN).

$$f(x_i) = e^{x_i} \{i = 1, 2, \dots, N\}$$

Multiple of these exponential values can be calculated with one accelerator instead of using one accelerator unit for each X_i . To reduce the required hardware resources for the softmax exponential function, a mathematical transformation would be useful. Each input value is split into an integer number Z_i and a fractional number V_i as below:

$$x_i = z_i + v_i$$

$$e^{x_i} = e^{z_i} * e^{v_i}$$


The second segment of this equation can be easily implemented with the exponential engine. To reduce the complexity of the hardware implementation of this equation, we use the base number 2 to take place of the base number e and the exponential function will be changed to:

$$e^{x_i} = 2^{u_i} * e^{v_i}$$

$$e^{x_i} = e^{v_i} \ll u_i$$

As can be seen, this equation can be implemented with a shifter that shifts e^{v_i} for u_i times. We are going to apply this transformation to the exponential in a wrapper around the exponential engine. Some other tasks are also included in the wrapper that are explained below:

Figure 4: Wrapper for exponential accelerator

 

- ➔ Referring to Figure 4, the wrapper receives single input in the form of a fractional value v_i , and an integer value u_i and a *start* signal from the processor.

- Considering the input values are within u_i and u_i+1 we can calculate n number of exponential in this range as follows:


$$e^{x_i} = \begin{cases} e^{2^i v_i} \ll u_i & \text{if } v_i < 1/2^{n-1} \\ e^{2^{n-1} v_i} \ll u_i & \text{if } u_i < x_i < u_i + 1 \end{cases}$$

In this experiment $n=4$. Based on these assumptions, 4 exponential values can be calculated. Four different values can be generated with the shift register unit by first registering the value of v_i and then shifting its value one bit to the left for each exponential calculation.

- The controller is responsible for generating the *load* and *shift enable* signals for the shift register, the *start* signal for the exponential engine, and the *load* signal for the u_i -register. The exponential engine should start each calculation when the previous one is completely done. For this purpose *engdone* is fed to the controller and when done is asserted the controller generates a complete pulse on *engstart*. At the same time, the correct value of x should appear on the corresponding input of the exponential engine. For each exponential value estimation, the controller issues the *wrreq* signal for writing data to the FIFO. When all calculations are finished the controller sends a *done* signal on the wrapper output.
- For shifting the output of the exponential engine, a combinational shifter is required. The input of this shifter is the u_i value that is provided outside the wrapper. To store the value of u_i , a register called u_i -reg is used.
- When an exponential value is calculated then it should be stored in a FIFO so that when the CPU finishes its work it can retrieve all the results. As shown in the Figure 4, the FIFO has a *writereq* input and a *write data* for writing into the buffer

and a *readreq* for reading the outputs. Since we are limited to four calculations in this experiment the FIFO size would be four as well.

 Here is state diagram for module controller and Huffman code for its verilog:



```
always @(*) begin
    ns = 3'b0;
    case (ps)
        IDLE: ns = start ? WAIT : IDLE;
        WAIT: ns = start ? WAIT : START;
        START: ns = CALC;
        CALC: ns = eng_done ? WRITE : CALC;
        WRITE: ns = count < 2'b11 ? START : DONE;
        DONE: ns = IDLE;
        default: ns = IDLE;
    endcase
end

always @(posedge clk, posedge rst) begin
    if(rst) count = 2'b0;
    else if(cnt) count = count + 1;
end

assign ldu = ps == WAIT;
assign ldx = ps == WAIT;
assign wr_req = ps == WRITE;
assign shl = ps == WRITE;
assign eng_start = ps == START;
assign done = ps == DONE;
assign cnt = ps == WRITE;
endmodule
```

In the next page you can see Verilog code for wrapper shown in figure 4 includes 5 component:

- 1-controller
- 2-combinational shift
- 3-Ui register
- 4-exponential unit
- 5-shift register


```





module Wrapper(clk, rst, start, v, u, done, wr_req, wr_data);
input clk, rst, start;
input[4:0] v;
input[1:0] u;
output done, wr_req;
output[20:0] wr_data;

wire ldx, ldu, shl, eng_start, eng_done;
wire[15:0] shreg_out, frac;
wire[1:0] int, ureg_out;

Controller controller(.clk(clk), .rst(rst), .wr_req(wr_req), .ldx(ldx), .ldu(ldu), .shl(shl), .eng_start(eng_start), .done(done), .
Shifting sh_reg(.clk(clk), .rst(rst), .ld(ldx), .sh(shl), .data(3'b0, v, 8'b0), .out(shreg_out));
Reg ureg(.clk(clk), .rst(rst), .ld(ldu), .data(u), .out(ureg_out));
exponential exp(.clk(clk), .rst(rst), .start(eng_start), .x(shreg_out), .done(eng_done), .intpart(int), .fracpart(frac));
ComShift comb_shift(.frac(frac), .int(int), .sh(ureg_out), .out(wr_data));
endmodule

```

    
And you can see our output on board LED is same as wave we got in Modelsim:



And LEDs for stack *full* and *done* signal be 1:




And this is our testbench result:

 

FPGA design

At last part we simulate this module with same input as Modelsim and see result with LED on board

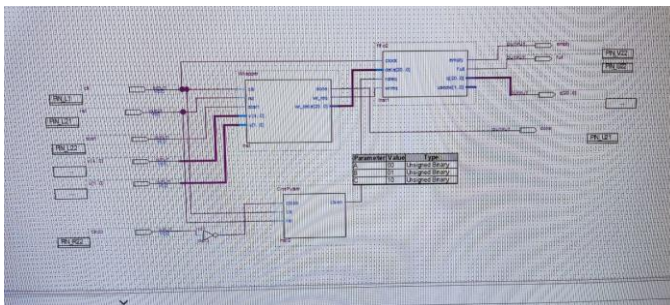First we build symbol of each component of wrapper and connect internal bus together:



And in next part we assign switch pins to our inputs and LED pins to done and FIFO full signal and other remained LEDs to MSB of our output:

Change View								
<div><div>Pin</div><div>IO Bank</div><div>WDF Group</div><div>I/O Standard</div><div>Reserved</div><div>Current Strength</div><div>Differential Pair</div></div>								
Node Name	Direction	Location	IO Bank	WDF Group	I/O Standard	Reserved	Current Strength	Differential Pair
u000	Output	PIN_301	0	RL_00	3.3V1V default	2mA (default)		
u001	Output	PIN_302	0	RL_00	3.3V1V default	2mA (default)		
u002	Output	PIN_303	0	RL_00	3.3V1V default	2mA (default)		
u003	Output	PIN_304	0	RL_00	3.3V1V default	2mA (default)		
u004	Output	PIN_305	0	RL_00	3.3V1V default	2mA (default)		
u005	Output	PIN_306	0	RL_00	3.3V1V default	2mA (default)		
u006	Output	PIN_307	0	RL_00	3.3V1V default	2mA (default)		
u007	Output	PIN_308	0	RL_00	3.3V1V default	2mA (default)		
u008	Output	PIN_309	0	RL_00	3.3V1V default	2mA (default)		
u009	Input	PIN_310	0	RL_00	3.3V1V default	2mA (default)		
u010	Input	PIN_311	0	RL_00	3.3V1V default	2mA (default)		
u011	Input	PIN_312	0	RL_00	3.3V1V default	2mA (default)		
u012	Input	PIN_313	0	RL_00	3.3V1V default	2mA (default)		
u099	Input	PIN_400	0	RL_00	3.3V1V default	2mA (default)		
u100	Input	PIN_401	0	RL_00	3.3V1V default	2mA (default)		
u101	Input	PIN_402	0	RL_00	3.3V1V default	2mA (default)		
u102	Input	PIN_403	0	RL_00	3.3V1V default	2mA (default)		
u103	Input	PIN_404	0	RL_00	3.3V1V default	2mA (default)		
u104	Input	PIN_405	0	RL_00	3.3V1V default	2mA (default)		
u105	Input	PIN_406	0	RL_00	3.3V1V default	2mA (default)		
u106	Input	PIN_407	0	RL_00	3.3V1V default	2mA (default)		
u107	Input	PIN_408	0	RL_00	3.3V1V default	2mA (default)		
u108	Input	PIN_409	0	RL_00	3.3V1V default	2mA (default)		
u109	Input	PIN_410	0	RL_00	3.3V1V default	2mA (default)		
u110	Input	PIN_411	0	RL_00	3.3V1V default	2mA (default)		
u111	Input	PIN_412	0	RL_00	3.3V1V default	2mA (default)		
u112	Input	PIN_413	0	RL_00	3.3V1V default	2mA (default)		
u113	Input	PIN_414	0	RL_00	3.3V1V default	2mA (default)		
u114	Input	PIN_415	0	RL_00	3.3V1V default	2mA (default)		
u115	Input	PIN_416	0	RL_00	3.3V1V default	2mA (default)		
u116	Input	PIN_417	0	RL_00	3.3V1V default	2mA (default)		
u117	Input	PIN_418	0	RL_00	3.3V1V default	2mA (default)		
u118	Input	PIN_419	0	RL_00	3.3V1V default	2mA (default)		
u119	Input	PIN_420	0	RL_00	3.3V1V default	2mA (default)		
u120	Input	PIN_421	0	RL_00	3.3V1V default	2mA (default)		
u121	Input	PIN_422	0	RL_00	3.3V1V default	2mA (default)		
u122	Input	PIN_423	0	RL_00	3.3V1V default	2mA (default)		
u123	Input	PIN_424	0	RL_00	3.3V1V default	2mA (default)		
u124	Input	PIN_425	0	RL_00	3.3V1V default	2mA (default)		
u125	Input	PIN_426	0	RL_00	3.3V1V default	2mA (default)		
u126	Input	PIN_427	0	RL_00	3.3V1V default	2mA (default)		
u127	Input	PIN_428	0	RL_00	3.3V1V default	2mA (default)		
u128	Input	PIN_429	0	RL_00	3.3V1V default	2mA (default)		
u129	Input	PIN_430	0	RL_00	3.3V1V default	2mA (default)		
u130	Input	PIN_431	0	RL_00	3.3V1V default	2mA (default)		
u131	Input	PIN_432	0	RL_00	3.3V1V default	2mA (default)		
u132	Input	PIN_433	0	RL_00	3.3V1V default	2mA (default)		
u133	Input	PIN_434	0	RL_00	3.3V1V default	2mA (default)		
u134	Input	PIN_435	0	RL_00	3.3V1V default	2mA (default)		
u135	Input	PIN_436	0	RL_00	3.3V1V default	2mA (default)		
u136	Input	PIN_437	0	RL_00	3.3V1V default	2mA (default)		
u137	Input	PIN_438	0	RL_00	3.3V1V default	2mA (default)		
u138	Input	PIN_439	0	RL_00	3.3V1V default	2mA (default)		
u139	Input	PIN_440	0	RL_00	3.3V1V default	2mA (default)		
u140	Input	PIN_441	0	RL_00	3.3V1V default	2mA (default)		
u141	Input	PIN_442	0	RL_00	3.3V1V default	2mA (default)		
u142	Input	PIN_443	0	RL_00	3.3V1V default	2mA (default)		
u143	Input	PIN_444	0	RL_00	3.3V1V default	2mA (default)		
u144	Input	PIN_445	0	RL_00	3.3V1V default	2mA (default)		
u145	Input	PIN_446	0	RL_00	3.3V1V default	2mA (default)		
u146	Input	PIN_447	0	RL_00	3.3V1V default	2mA (default)		
u147	Input	PIN_448	0	RL_00	3.3V1V default	2mA (default)		
u148	Input	PIN_449	0	RL_00	3.3V1V default	2mA (default)		
u149	Input	PIN_450	0	RL_00	3.3V1V default	2mA (default)		
u150	Input	PIN_451	0	RL_00	3.3V1V default	2mA (default)		
u151	Input	PIN_452	0	RL_00	3.3V1V default	2mA (default)		
u152	Input	PIN_453	0	RL_00	3.3V1V default	2mA (default)		
u153	Input	PIN_454	0	RL_00	3.3V1V default	2mA (default)		
u154	Input	PIN_455	0	RL_00	3.3V1V default	2mA (default)		
u155	Input	PIN_456	0	RL_00	3.3V1V default	2mA (default)		
u156	Input	PIN_457	0	RL_00	3.3V1V default	2mA (default)		
u157	Input	PIN_458	0	RL_00	3.3V1V default	2mA (default)		
u158	Input	PIN_459	0	RL_00	3.3V1V default	2mA (default)		
u159	Input	PIN_460	0	RL_00	3.3V1V default	2mA (default)		
u160	Input	PIN_461	0	RL_00	3.3V1V default	2mA (default)		
u161	Input	PIN_462	0	RL_00	3.3V1V default	2mA (default)		
u162	Input	PIN_463	0	RL_00	3.3V1V default	2mA (default)		
u163	Input	PIN_464	0	RL_00	3.3V1V default	2mA (default)		
u164	Input	PIN_465	0	RL_00	3.3V1V default	2mA (default)		
u165	Input	PIN_466	0	RL_00	3.3V1V default	2mA (default)		
u166	Input	PIN_467	0	RL_00	3.3V1V default	2mA (default)		
u167	Input	PIN_468	0	RL_00	3.3V1			